

# Advanced Boolean Logic


Prof. James L. Frankel  
Harvard University

Version of 10:13 AM 2-Dec-2021  
Copyright © 2021, 2020, 2017 James L. Frankel. All rights reserved.

# Half-Adder

A	B	S (Sum)	C (Carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Encapsulation of Half-Adder

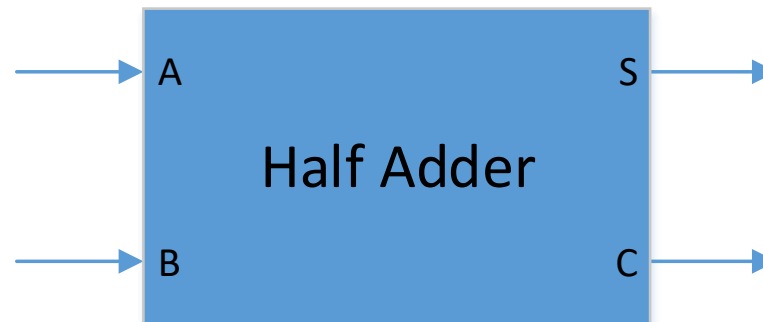

# Full-Adder

A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-Adder: All Zero Inputs

A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-Adder: Only One Input is High

A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-Adder: Exactly Two Inputs are High


A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-Adder: All Three Inputs are High


A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Encapsulation of Full-Adder

 

# Four-bit Adder Built from Full Adders

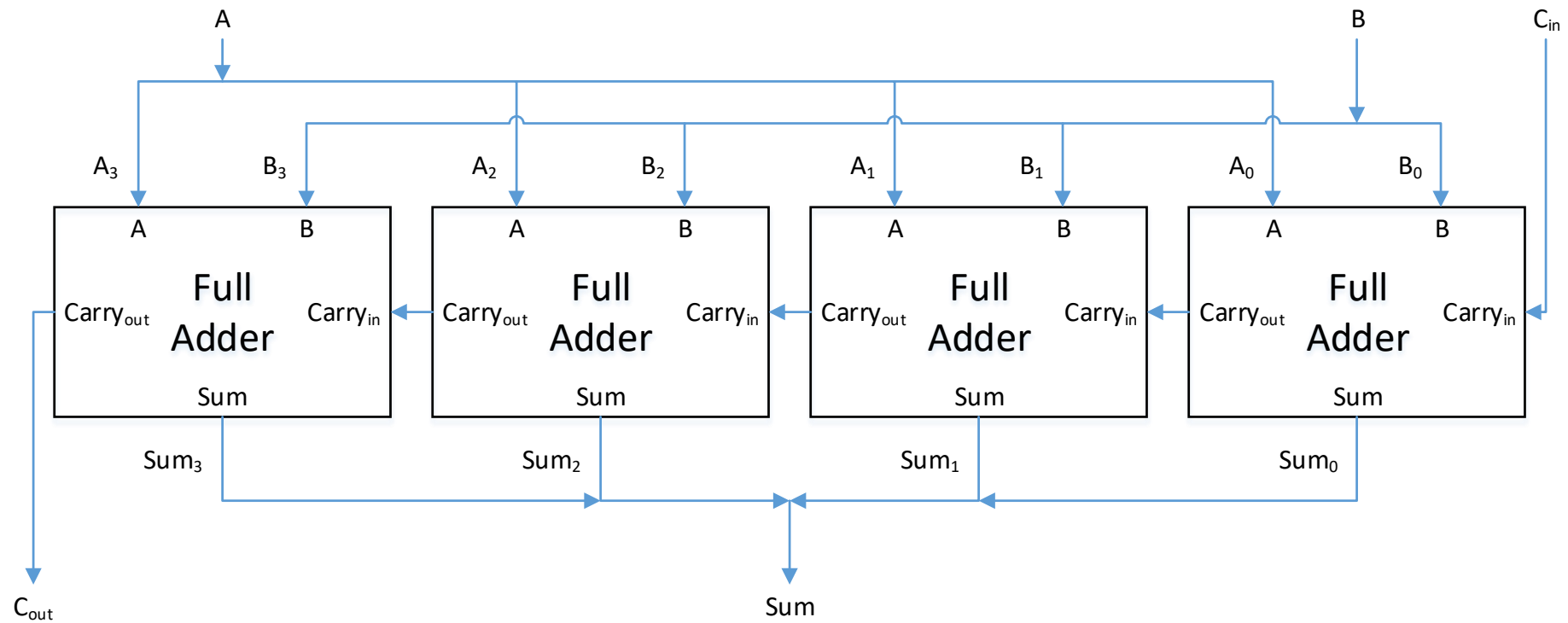

# Sum-of-Products Form

- OR is like SUM (addition)
- AND is like PRODUCT (multiplication)
- So, a sum-of-products Boolean formula has any of the following forms:
  - $(A \text{ AND } B) \text{ OR } (C \text{ AND } D) \text{ OR } (E \text{ AND } F)$
  - $(A \ \& \ B) \ | \ (C \ \& \ D) \ | \ (E \ \& \ F)$
  - $(A \ \wedge \ B) \ \vee \ (C \ \wedge \ D) \ \vee \ (E \ \wedge \ F)$
  - $(A \cdot B) + (C \cdot D) + (E \cdot F)$
  - $(AB) + (CD) + (EF)$
  - $AB + CD + EF$


# Sum-of-Products: Start with the Truth Table

A	B	R
0	0	$R_0$
0	1	$R_1$
1	0	$R_2$
1	1	$R_3$

- Generalized Formula:  $R = \overline{A}\overline{B}R_0 + \overline{A}BR_1 + A\overline{B}R_2 + ABR_3$
 
# Sum-of-Products: Could Draw Gates

- Generalized Formula:  $R = \overline{\overline{A}}\overline{B}R_0 + \overline{A}BR_1 + A\overline{B}R_2 + ABR_3$



# Sum-of-Products: With Specific Values for $R_0$ through $R_3$ , Terms are Removed and Simplified

A	B	R
0	0	$R_0 = 0$
0	1	$R_1 = 1$
1	0	$R_2 = 1$
1	1	$R_3 = 0$

- $R = \overline{A}\overline{B}0 + \overline{A}B1 + A\overline{B}1 + AB0$
- $R = \overline{A}B + A\overline{B}$

# Sum-of-Products: Observation

- The only terms that persist are those with 1 outputs
- So, we need only include those terms

# Sum-of-Products: Returning to the Full Adder

- Given the truth table,

A	B	Carry <sub>in</sub>	Sum	Carry <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- The sum-of-products formulae are


$$Sum = \overline{A}\overline{B}Carry_{in} + \overline{A}BCarry_{in} + \overline{A}B\overline{Carry}_{in} + ABCarry_{in}$$

$$Carry_{out} = \overline{A}BCarry_{in} + \overline{A}B\overline{Carry}_{in} + \overline{A}B\overline{Carry}_{in} + ABCarry_{in}$$



 
# Sum-of-Products: Full Adder Sum

$$Sum = \overline{\overline{A}}\overline{B}Carry_{in} + \overline{A}\overline{\overline{B}}\overline{Carry_{in}} + \overline{\overline{A}}\overline{B}Carry_{in} + \overline{A}\overline{\overline{B}}\overline{Carry_{in}}$$


 
# Sum-of-Products: Full Adder Carry<sub>out</sub>

$$Carry_{out} = \overline{A}B\overline{Carry_{in}} + A\overline{B}\overline{Carry_{in}} + \overline{A}B\overline{Carry_{in}} + ABCarry_{in}$$



# ALU (Arithmetic/Logic Unit)

- The ALU is the component in a CPU that can perform arithmetic and logic operations
- Usually accepts two multi-bit (word size) operands
  - Let's refer to them as **A** and **B**
- Usually produces a single multi-bit (word size) result
  - Let's refer to it as **R**
- The ALU can perform one of many functions
  - Let's refer to the input that selects the function as the **function**
- Usually also produces flags that indicate properties of the result
  - Is the result zero?
  - Is the result negative?
  - Was a Carry<sub>out</sub> produced in computing the result?
  - Did overflow occur in computing the result?

# ALU Operations

- Arithmetic operations might be
  - Addition
  - Subtraction
  - Addition plus 1
  - etc.
- Logic operations might be
  - NOT A
  - NOT B
  - AND
  - OR
  - NAND
  - NOR
  - XOR
  - EQV
  - etc.

# ALU Encapsulation

