

# Binary Logic Levels

Prof. James L. Frankel  
Harvard University

Version of 10:08 AM 2-Dec-2021  
Copyright © 2021, 2019, 2017, 2016 James L. Frankel. All rights reserved.

# Getting Started Rules

- All signals are *really analog* and not digital
- Logic circuits require direct current (DC) power to function
- Signals are represented by a direct current (DC) voltage
- The binary value zero (0) is represented by a low voltage and the binary value one (1) is represented by a high voltage
- Do not connect an output to another output
- There are a limited number of inputs than can be connected to a single output (for TTL, that number is usually ten)
  - This is referred to as the **fan-out**
- Signals exhibit noise and vary over time
- Do not depend on the value of a signal when it is possibly changing state from high to low or from low to high


# Power Supply to TTL Logic Circuits

- TTL is an acronym for Transistor-Transistor Logic
- TTL was the initial fundamental logic family used in digital Integrated Circuits (ICs)
- Supply Voltage = 5V DC
  - Called  $V_{CC}$  for bipolar junction transistor (BJT) (NPN and PNP transistor) logic families
- Ground = 0V DC
  - Called GND
  - Also called  $V_{EE}$  for bipolar junction transistor (BJT) (NPN and PNP transistor) logic families
- Elementary logic circuits are called “gates”
- Today, most circuits use CMOS logic


# Power Supply to CMOS Logic Circuits

- CMOS is an acronym for Complementary Metal-Oxide-Semiconductor
- Uses complementary pairs of P-type and N-type Metal Oxide Semiconductor Field Effect Transistors (MOSFETs)
- Supply Voltage = 5V DC, 3.3V DC (fairly common), 2.4V DC, 1.8V DC, 1.2V DC
  - Called  $V_{DD}$  for CMOS logic families
- Ground = 0V DC
  - Called  $V_{SS}$  for CMOS logic families
- We'll be examining voltage levels used by the TTL family in more detail


# Connections Among Logic Elements

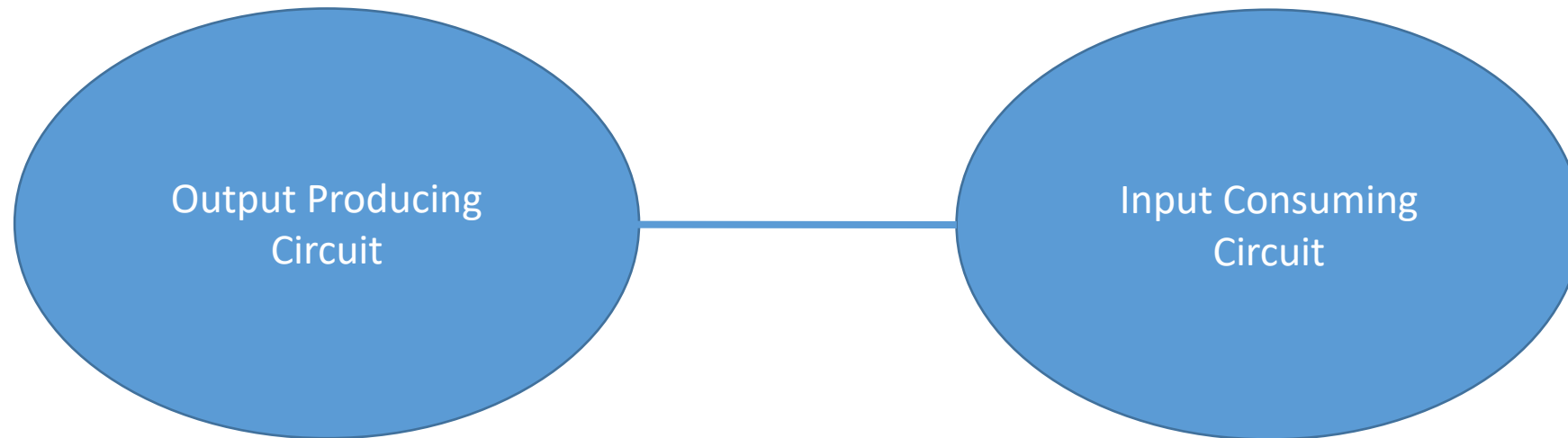


# Acceptable Input Voltages in TTL

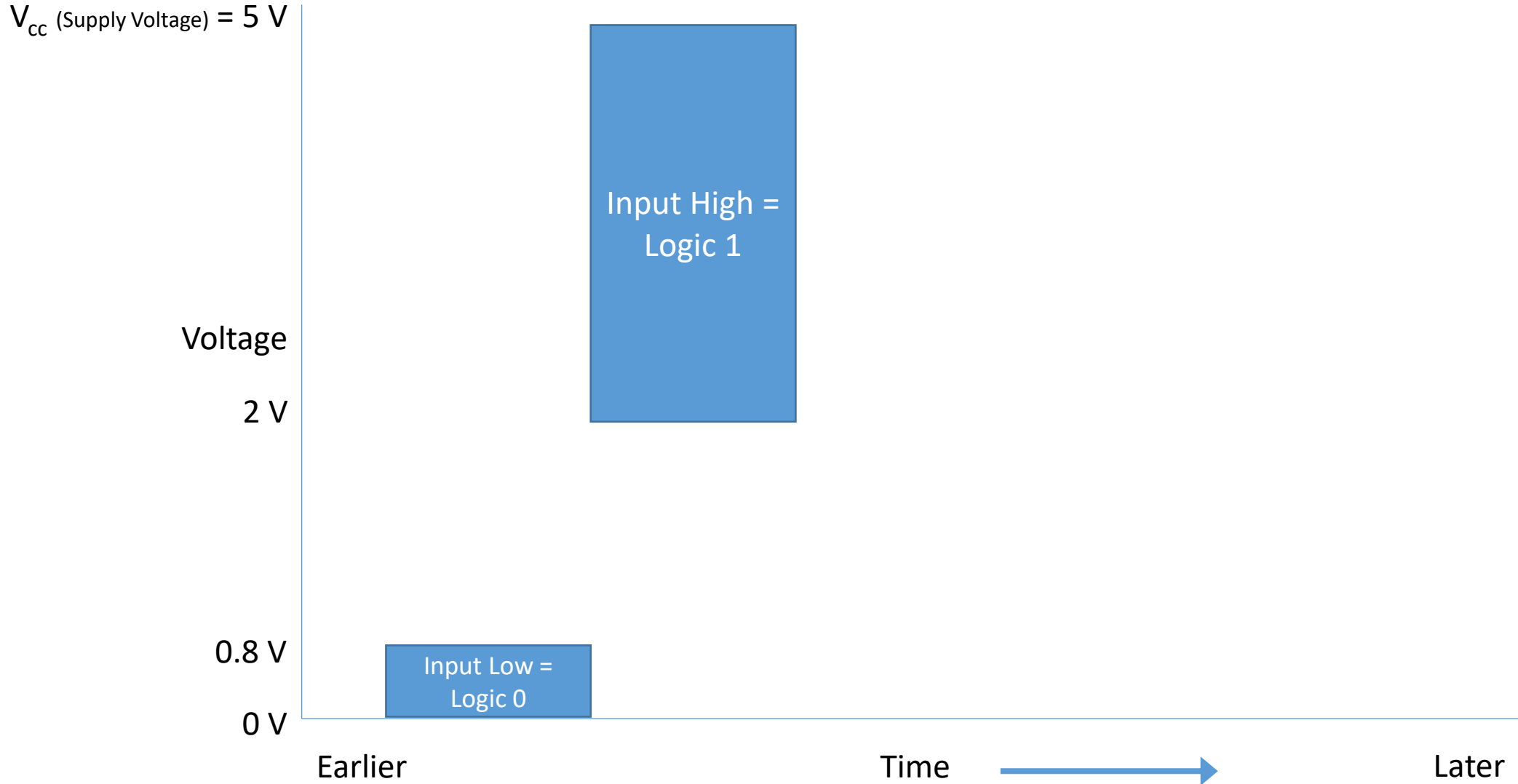

# Acceptable Output Voltages in TTL

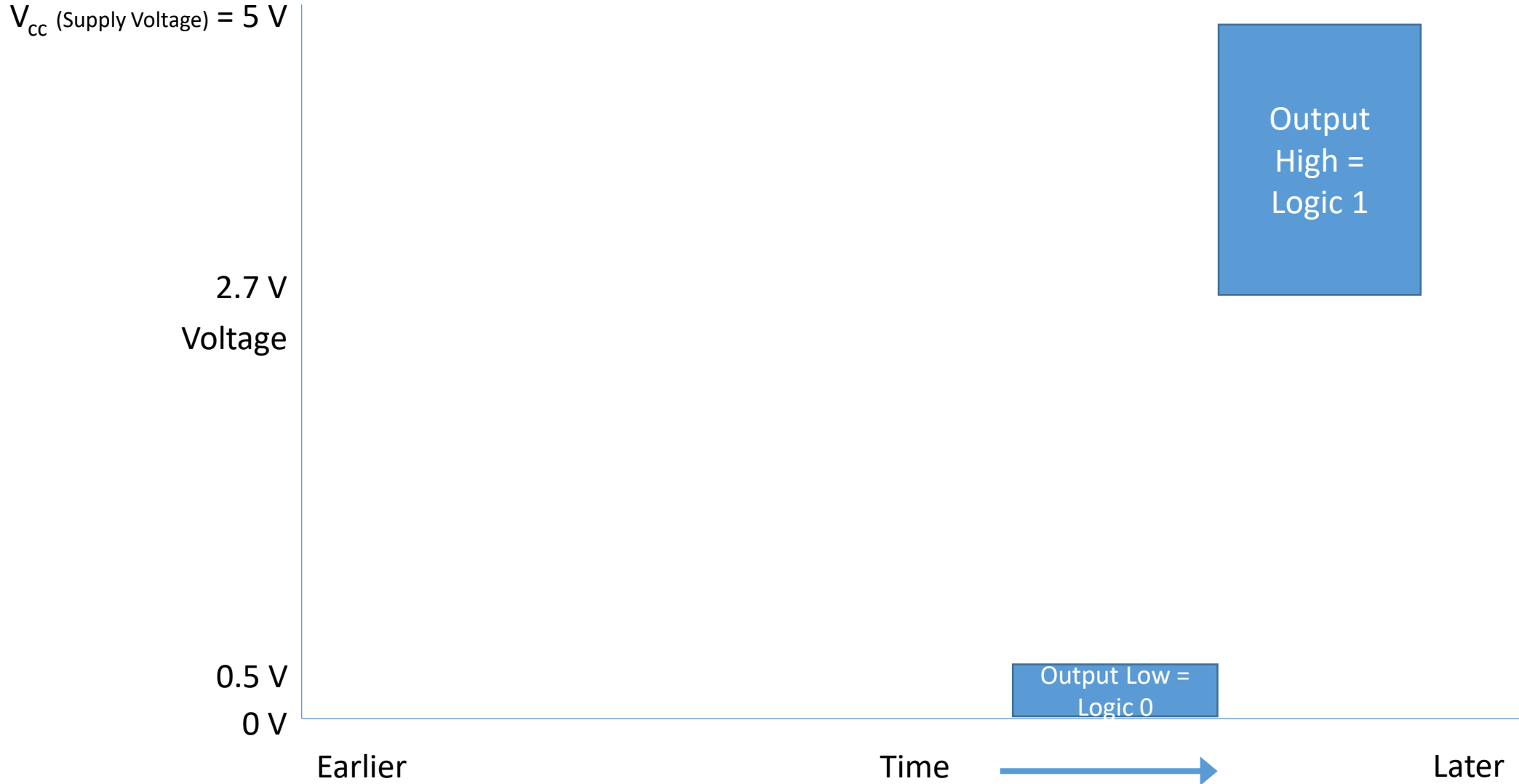


$V_{CC}$  (Supply Voltage) = 5 V

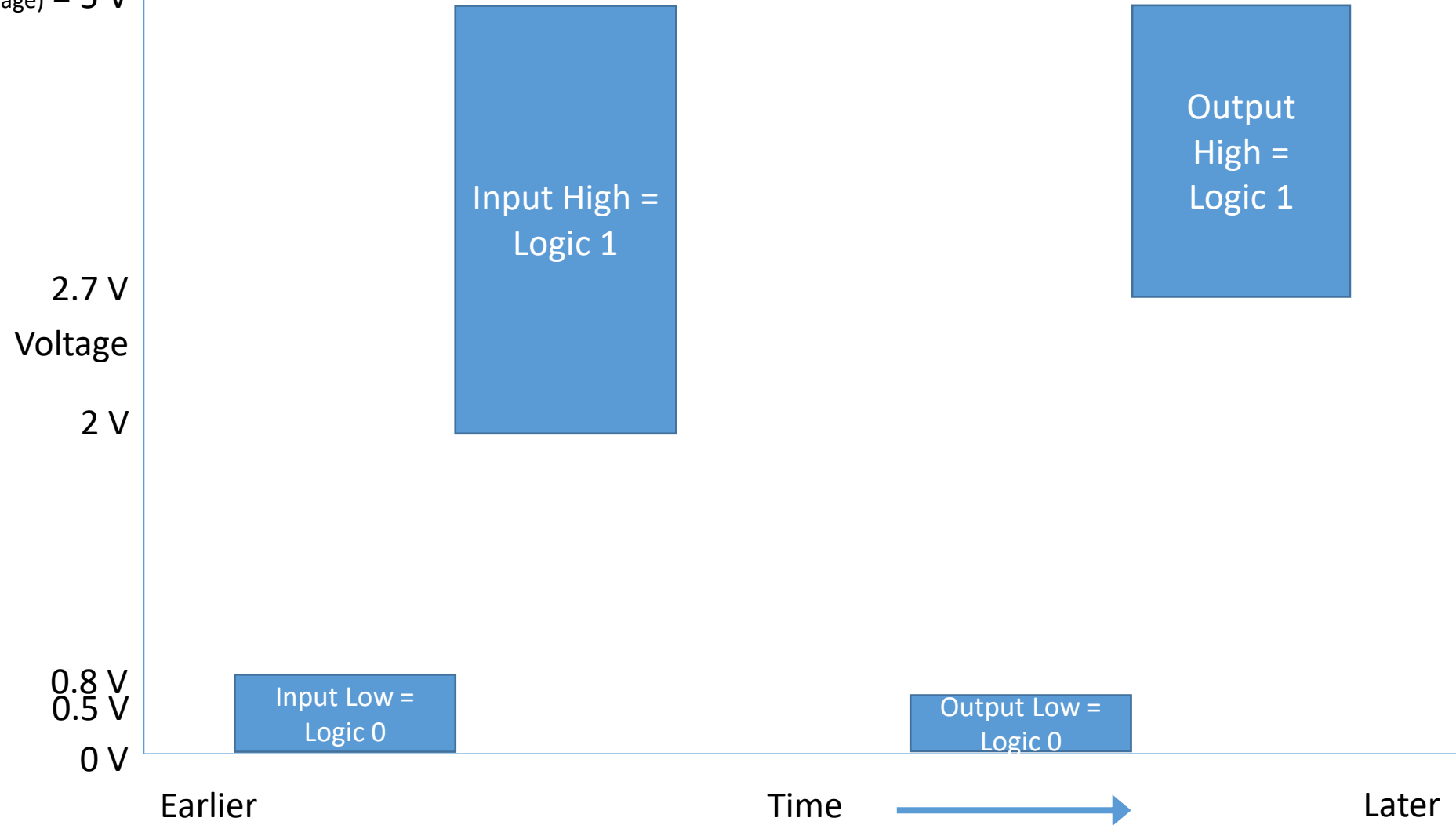




$V_{CC}$  (Supply Voltage) = 5 V

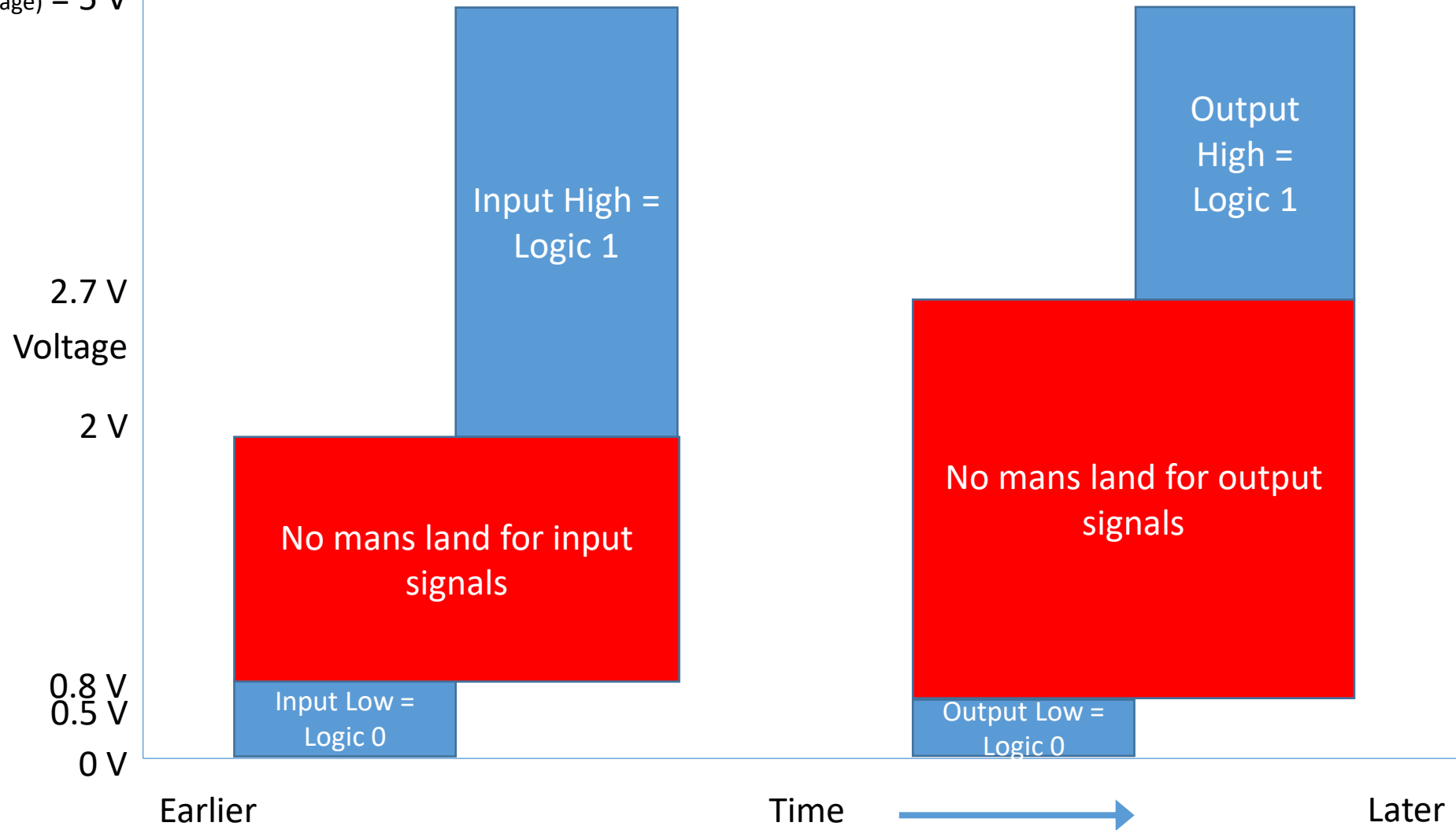

$V_{CC}$  (Supply Voltage) = 5 V

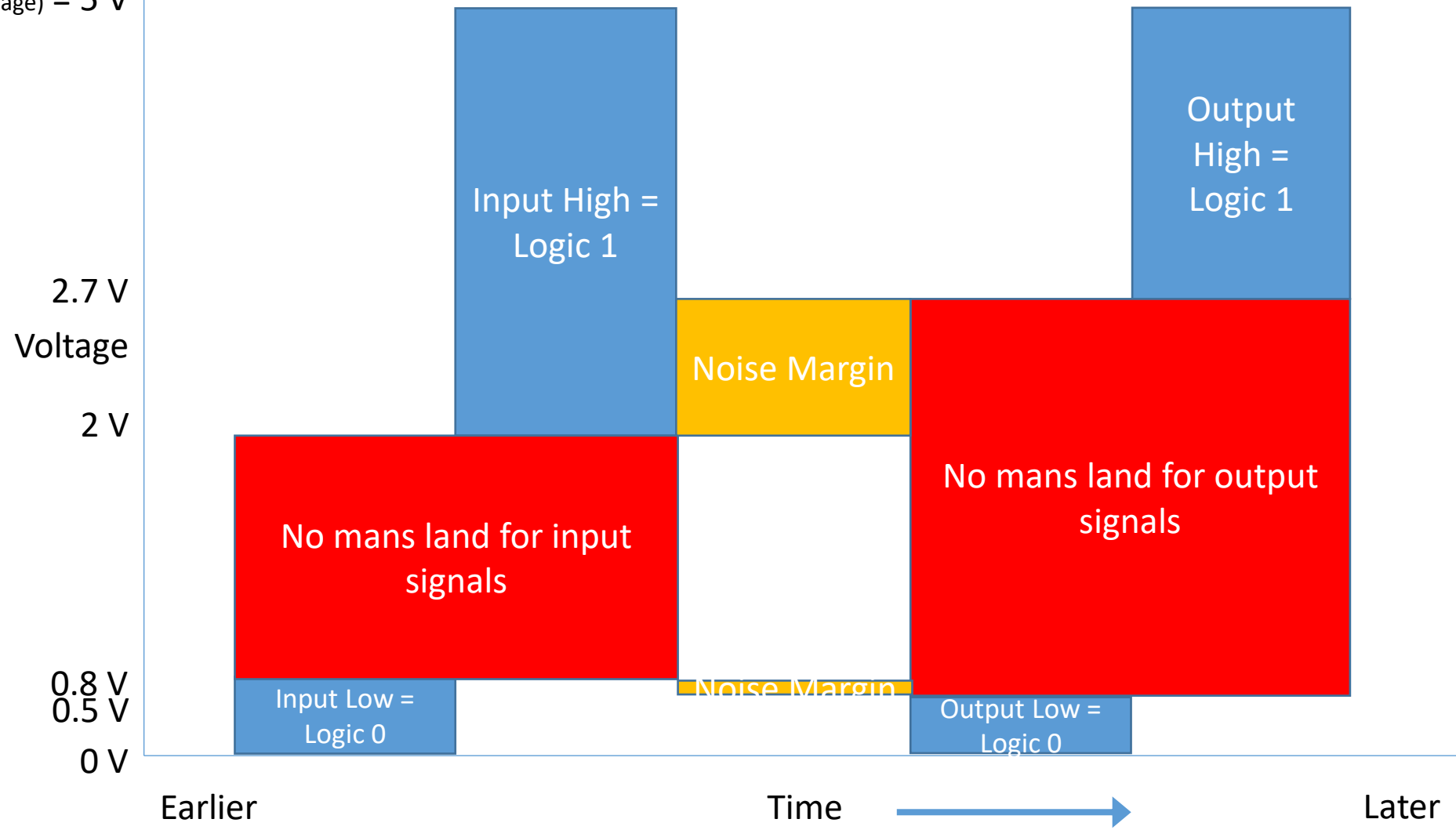

# Review of TTL Binary Logic Levels

- Supply Voltage =  $V_{CC} = 5V$
- Ground = GND = 0V
- Input Low Logic Levels: 0V – 0.8V
- Input High Logic Levels: 2V – 5V
- Output Low Logic Levels: 0V – 0.5V
- Output High Logic Levels: 2.7V – 5V