

# Pipelining

Prof. James L. Frankel  
Harvard University

Version of 11:11 PM 1-Dec-2021  
Copyright © 2021, 2020, 2019 James L. Frankel. All rights reserved.

# Single-Cycle CPU Implementation

- The clock cycle must be long enough to accommodate the longest instruction
- There is no overlapping of the execution of instructions
- With time-consuming instructions (floating point, memory access), the penalty is high

# Pipelining

- Decreases the average number of cycles per instruction (CPI) – throughput
- Does not decrease the time for any single instruction – latency


# Memory Organization

- We will allow the assumption that there are “two” memories – one for instructions and one for data
- This is not *really* the case
- We will have an instruction cache and a data cache
  - These will create the illusion that we have two separate memories

# Instruction Set Design for Pipelining


- All instructions are the same length
  - x86 ISA has 1 to 15 bytes per instruction
- Small number of instruction formats
  - Operands can be fetched from registers before determining the instruction type
- Load/store architecture means that the EX (ALU) stage can compute the memory address
  - If operands could come from memory, then the memory access would need to precede the EX stage
- All memory accesses are aligned
  - Only a single memory access is required

# Data Path Split into Pipeline Stages

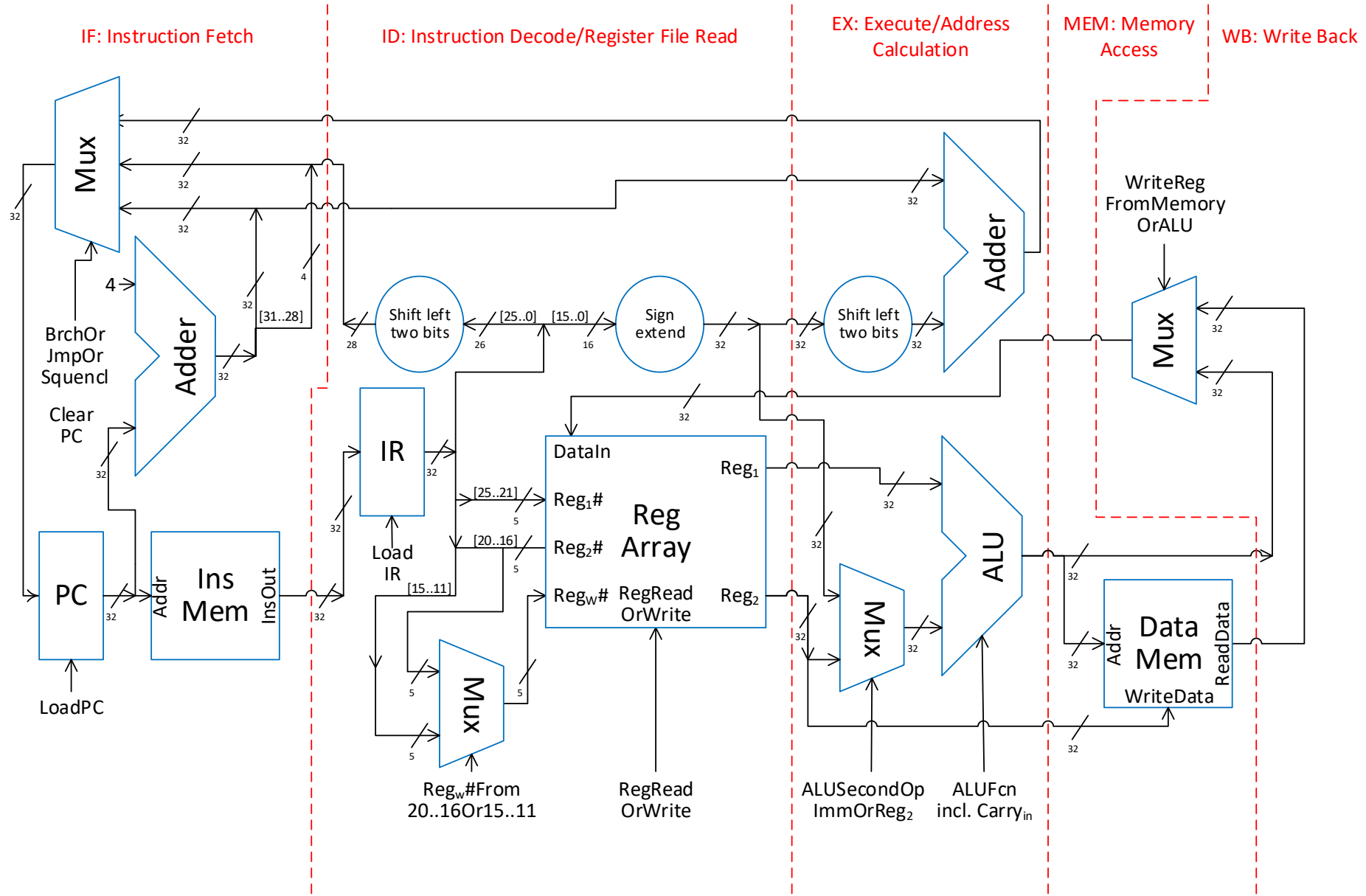


Right to Left Data Paths are Problematic



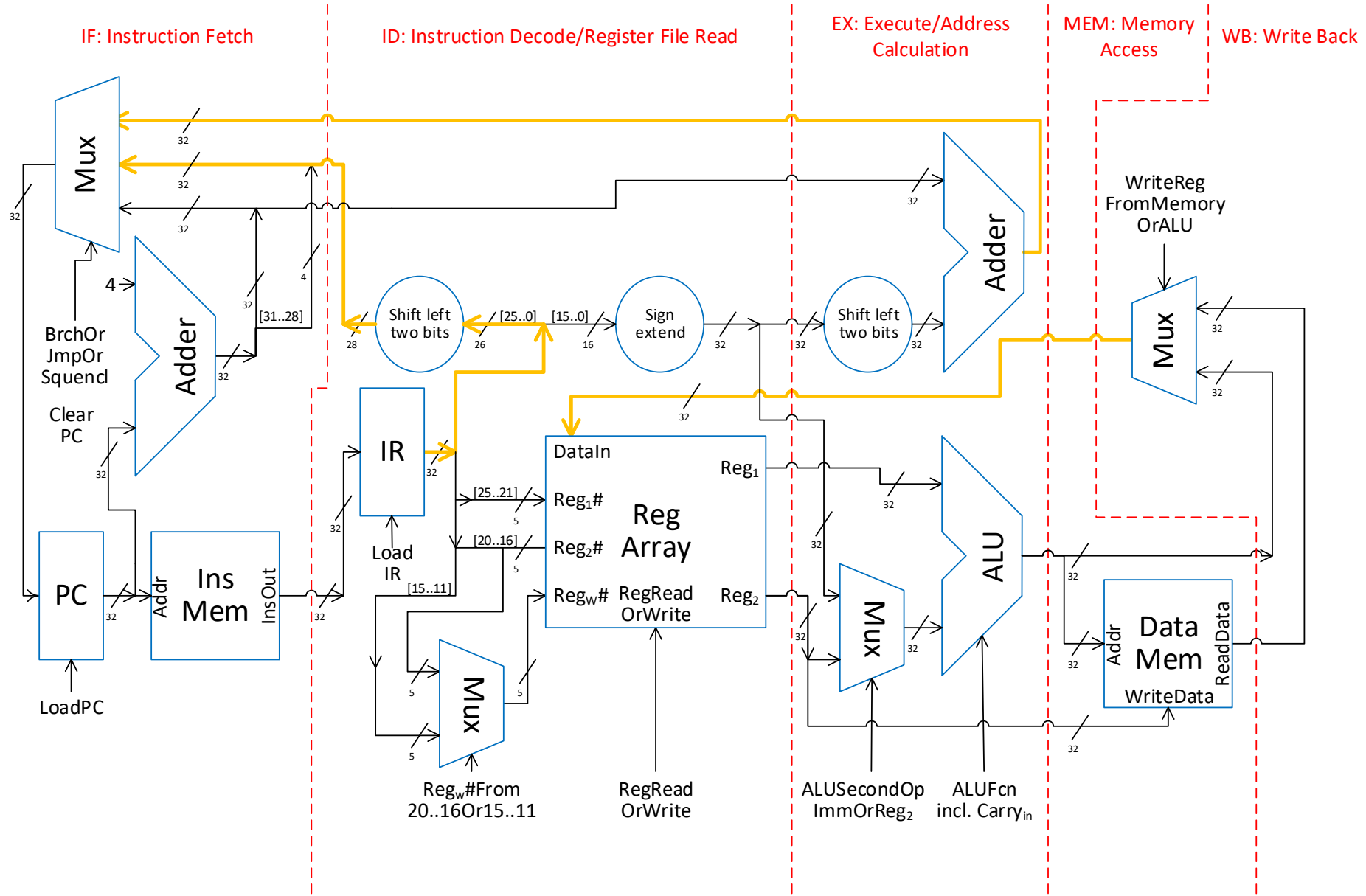


# Pipelining Three lw Instructions

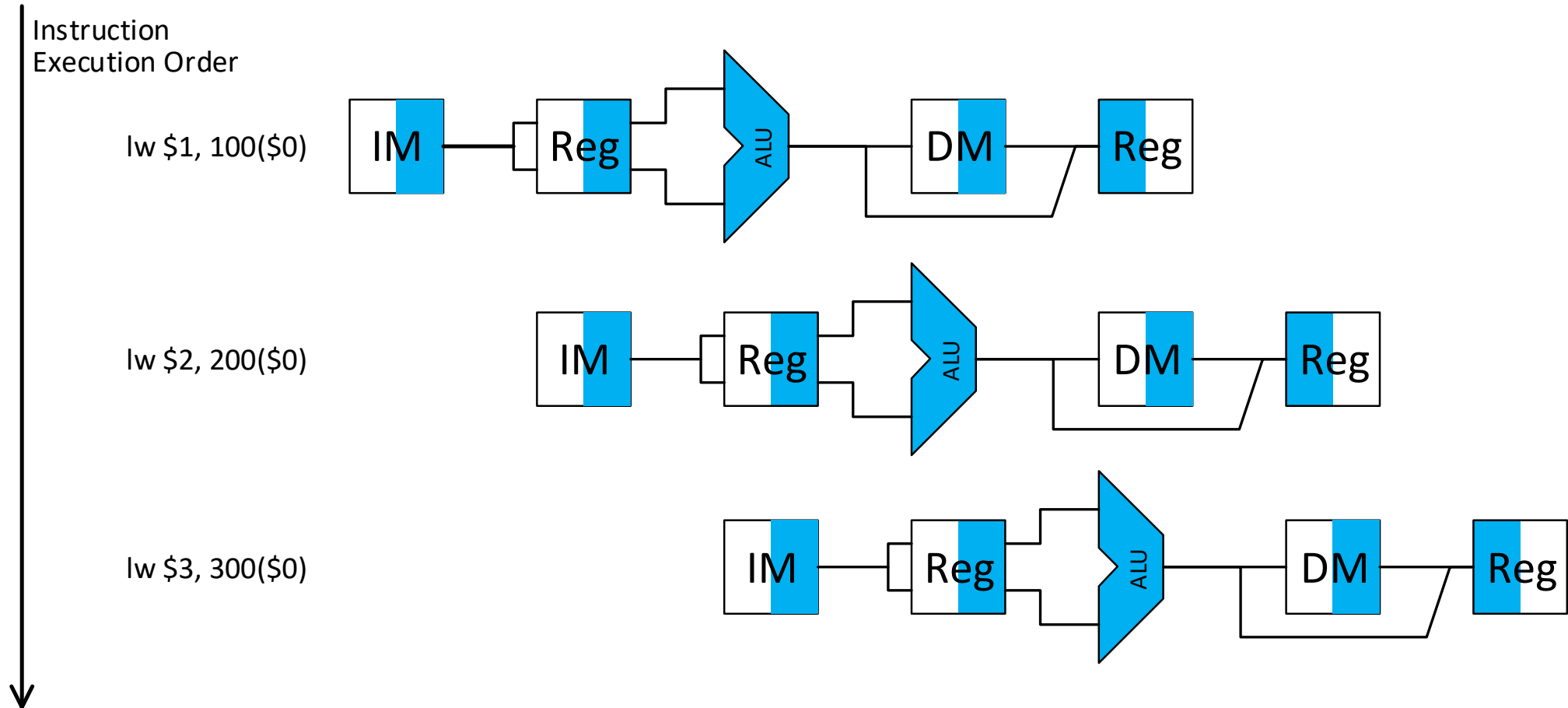

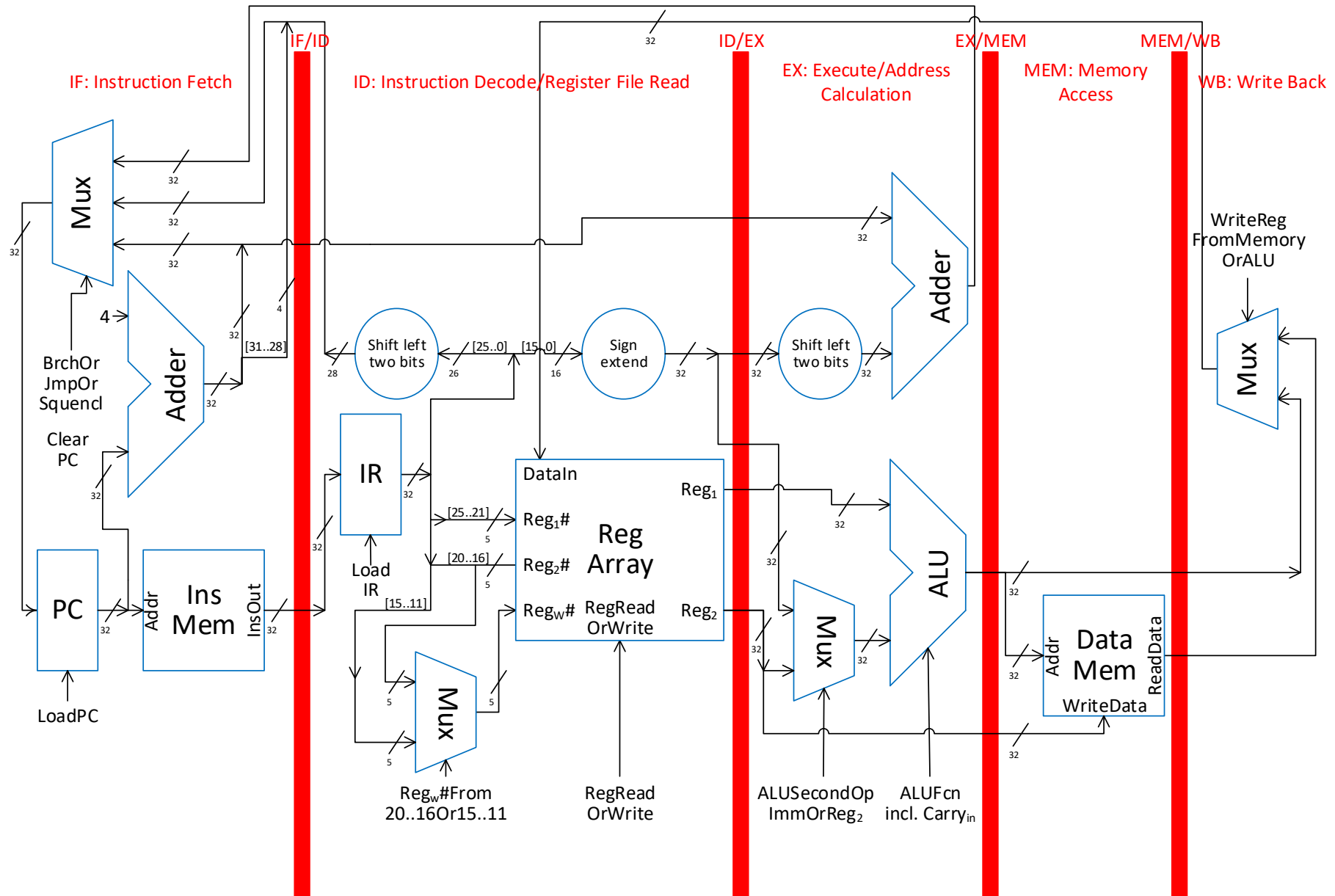
# Staging the Pipelined Data

- Add pipeline registers between stages
- Allows the pipeline stages to run independently within the same clock cycle




# lw Instruction in IF Pipeline Stage

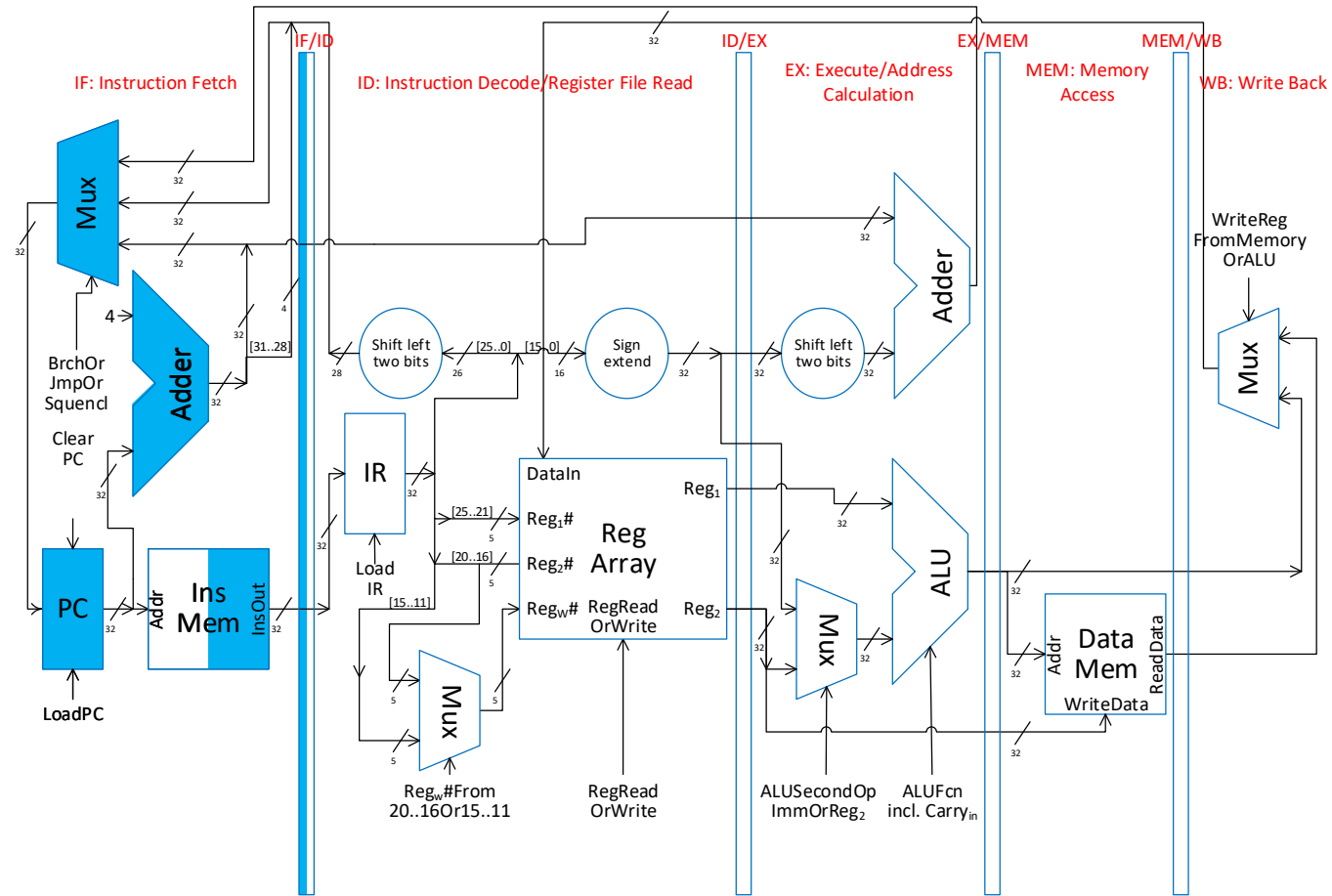


# ID (Instruction Decode) Stage

- No need to keep the IR as a register because the current instruction is stored in the IF/ID pipeline register

# lw Instruction in ID Pipeline Stage

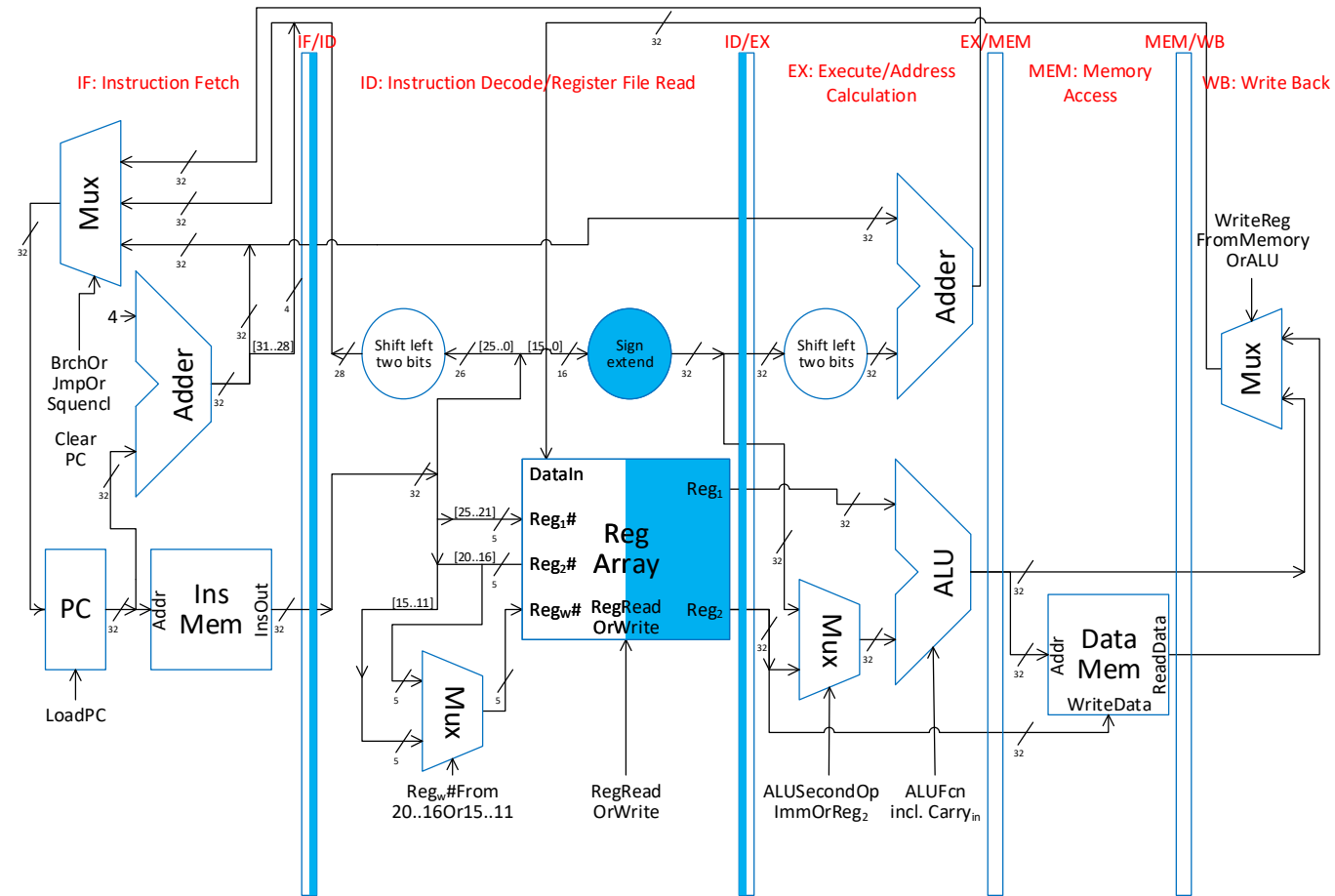


# lw Instruction in EX Pipeline Stage

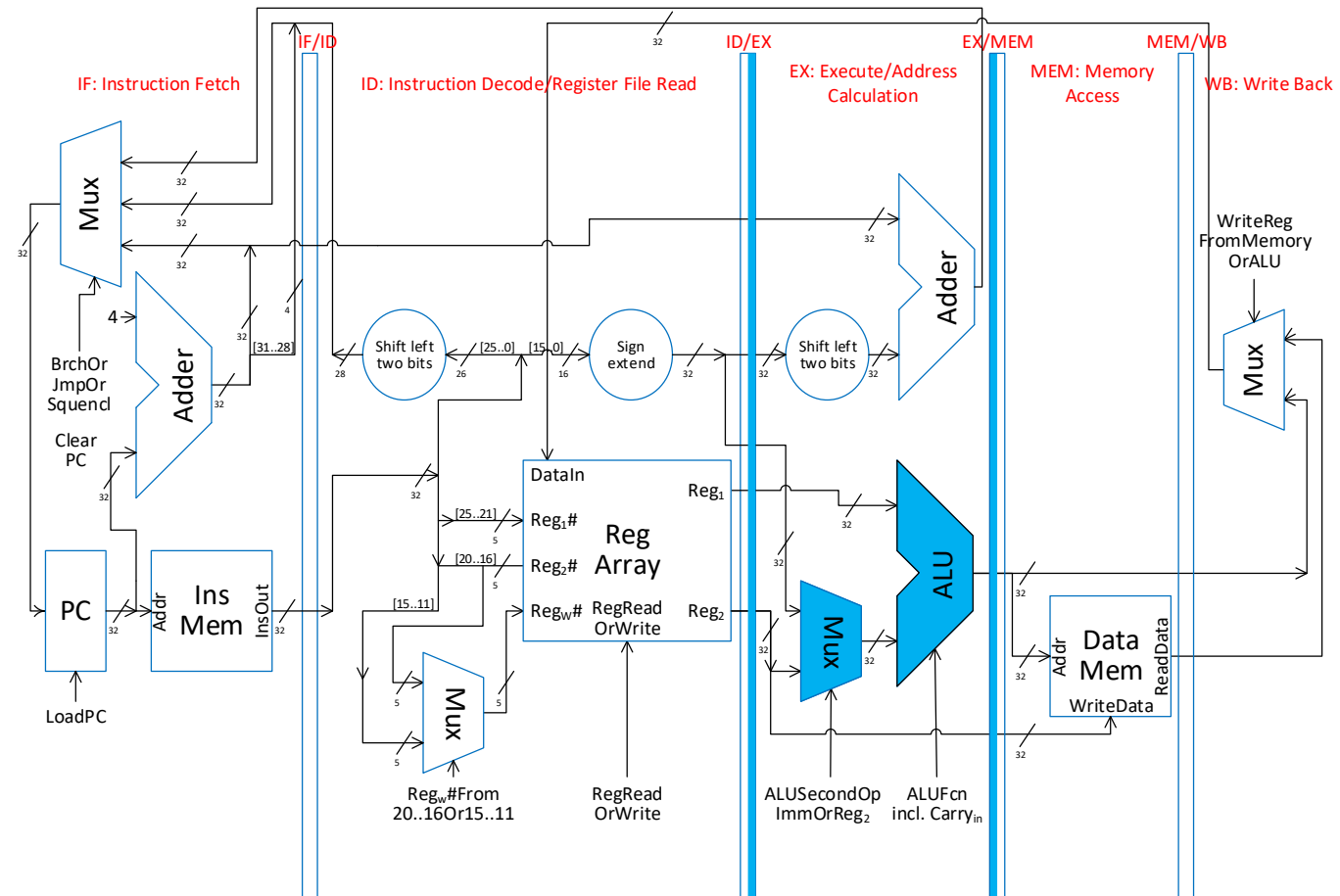




# lw Instruction in MEM Pipeline Stage

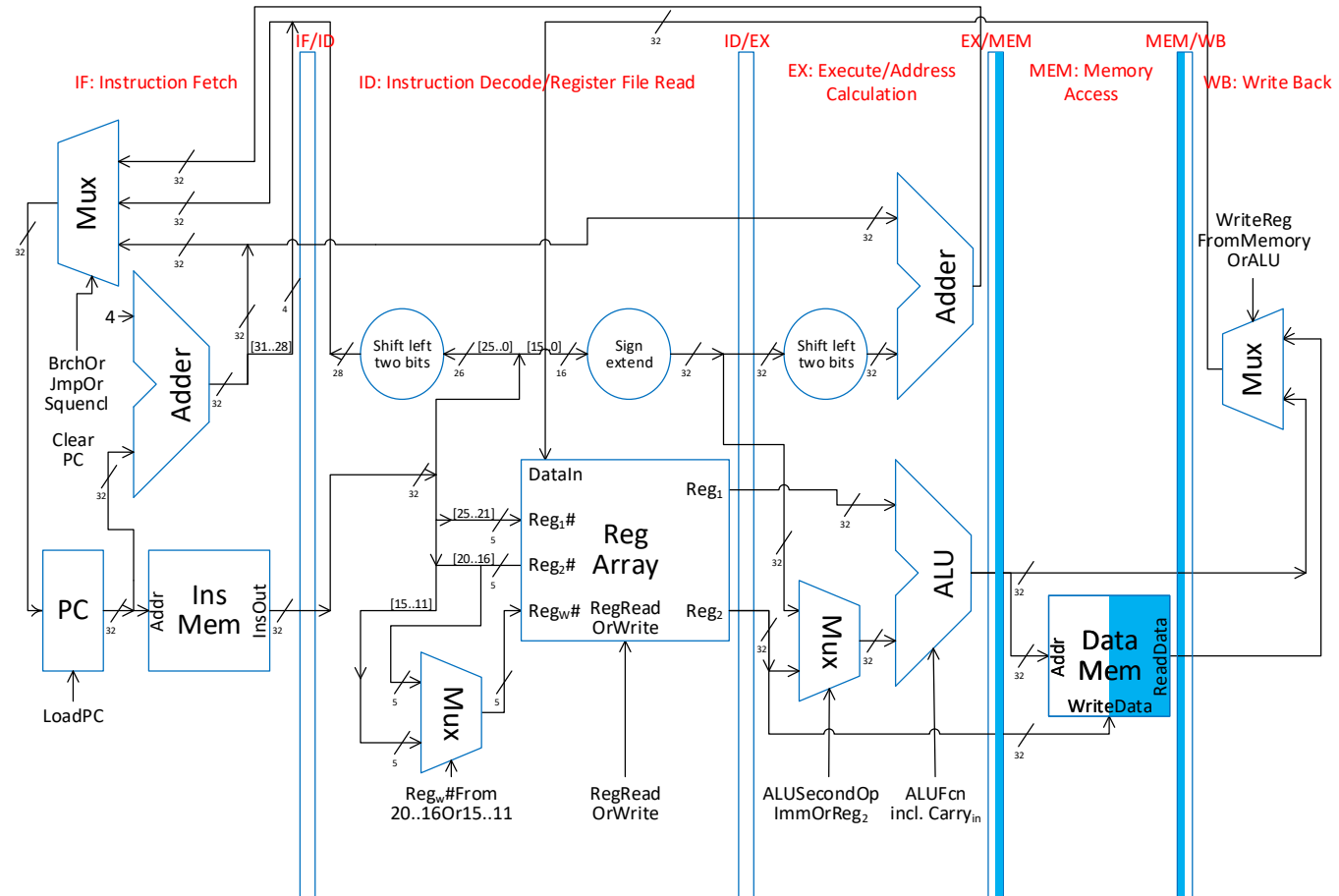


# lw Instruction in WB Pipeline Stage

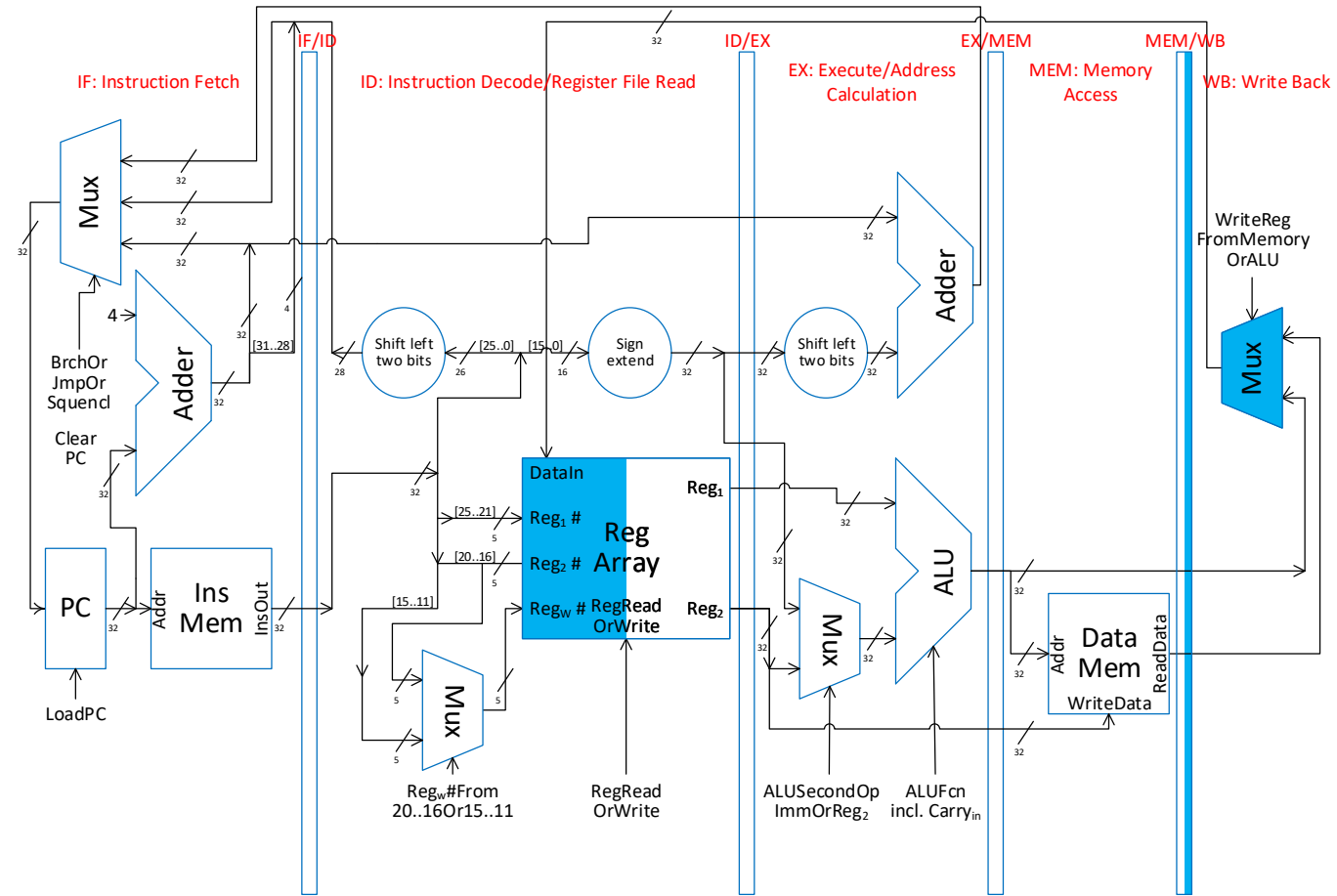


# Problem with lw in WB Pipeline Stage

- Unfortunately, the incorrect register is written in the WB stage
- The  $\text{Reg}_w\#$  is coming from the wrong pipeline stage!
- Let's correct the problem by keeping the  $\text{Reg}_w\#$  with the value that will be written to that register

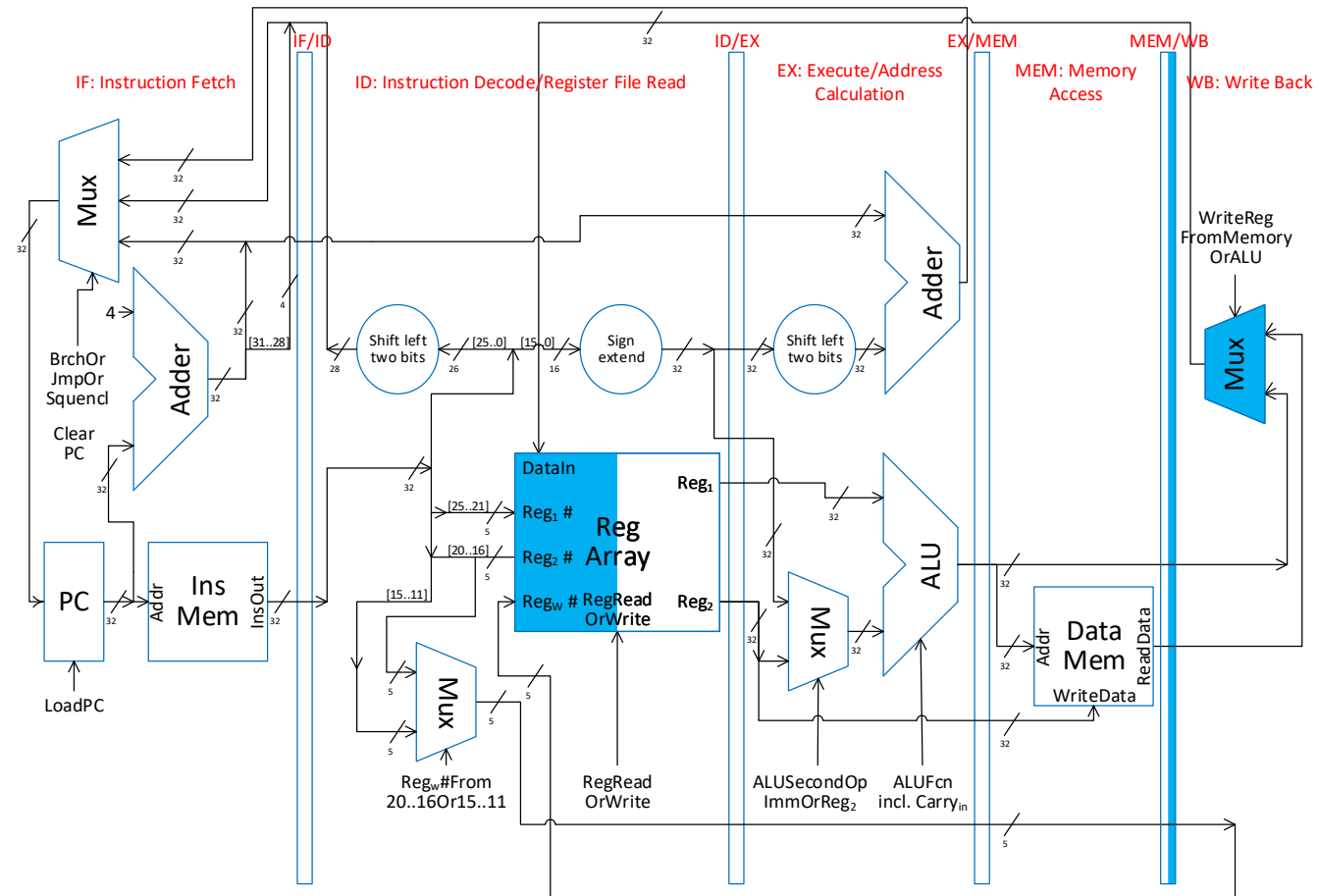
# Corrected Pipeline Diagram for lw Instruction in WB Pipeline Stage




# Executing an sw Instruction

 

# sw Instruction in MEM Pipeline Stage

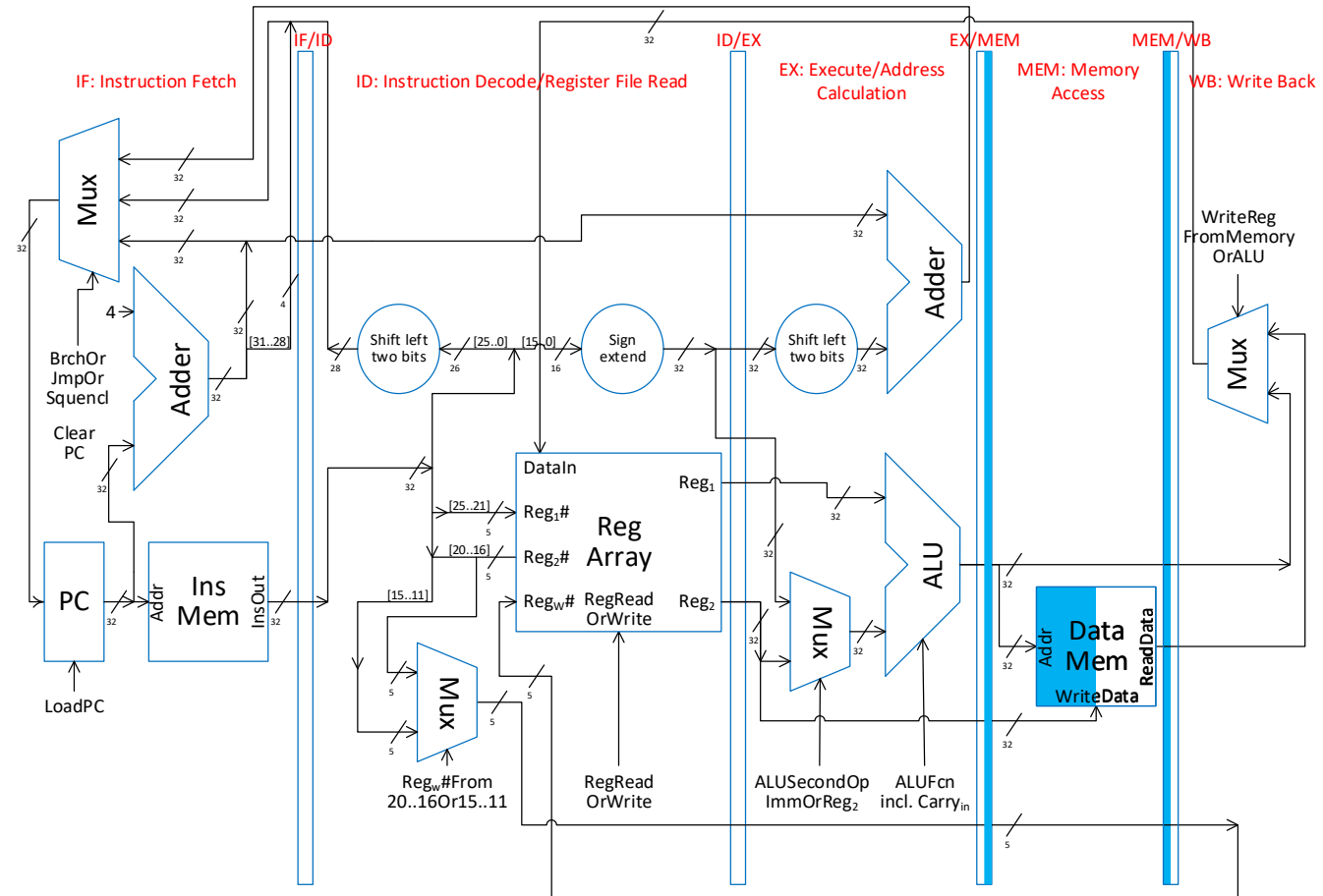

# sw Instruction in WB Pipeline Stage

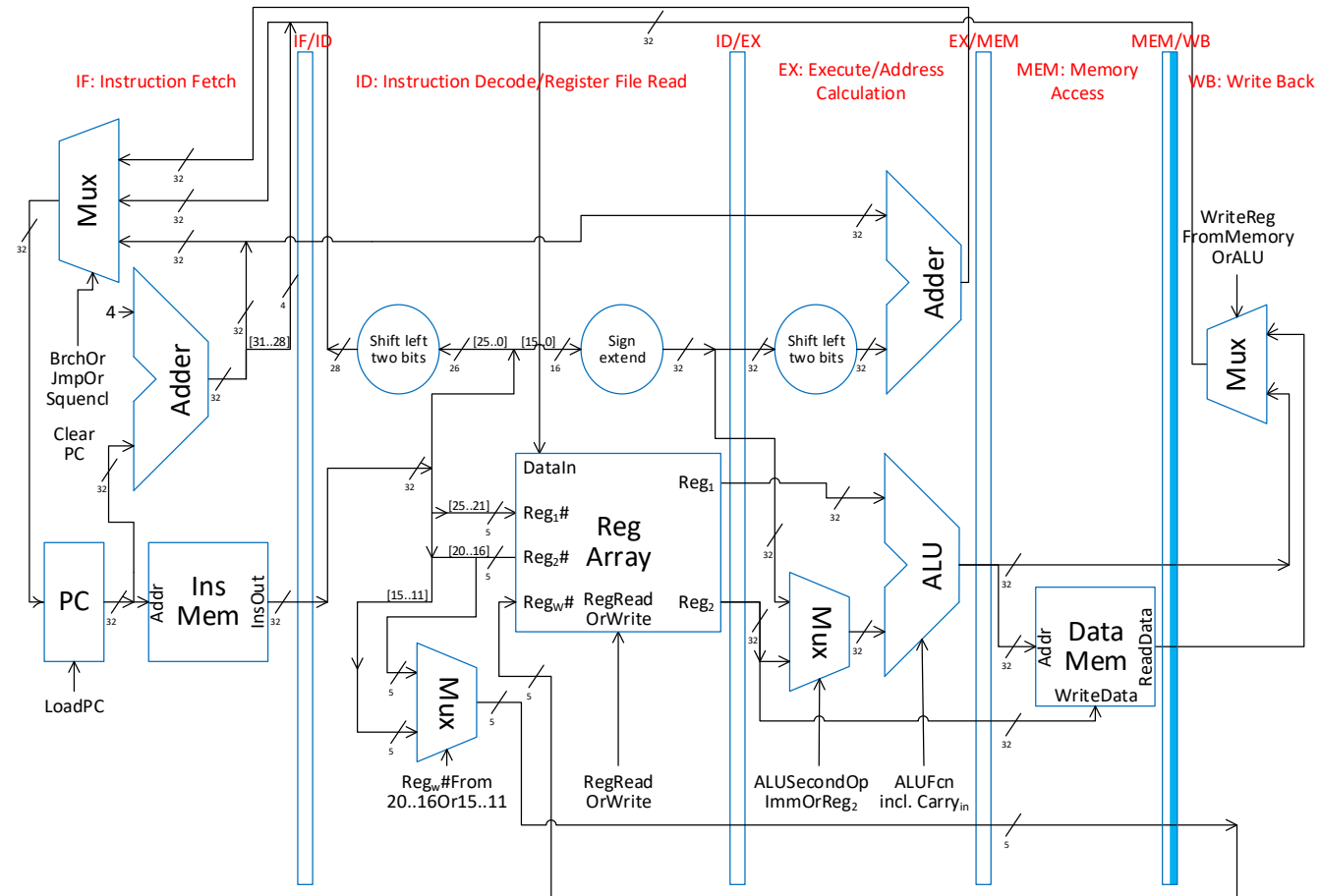

# Sequence of Instructions

- Imaging the pipelined execution of a sequence of five instructions:

lw     \$10, 20(\$1)

sub    \$11, \$2, \$3


add    \$12, \$3, \$4

lw     \$13, 24(\$1)


add    \$14, \$5, \$6


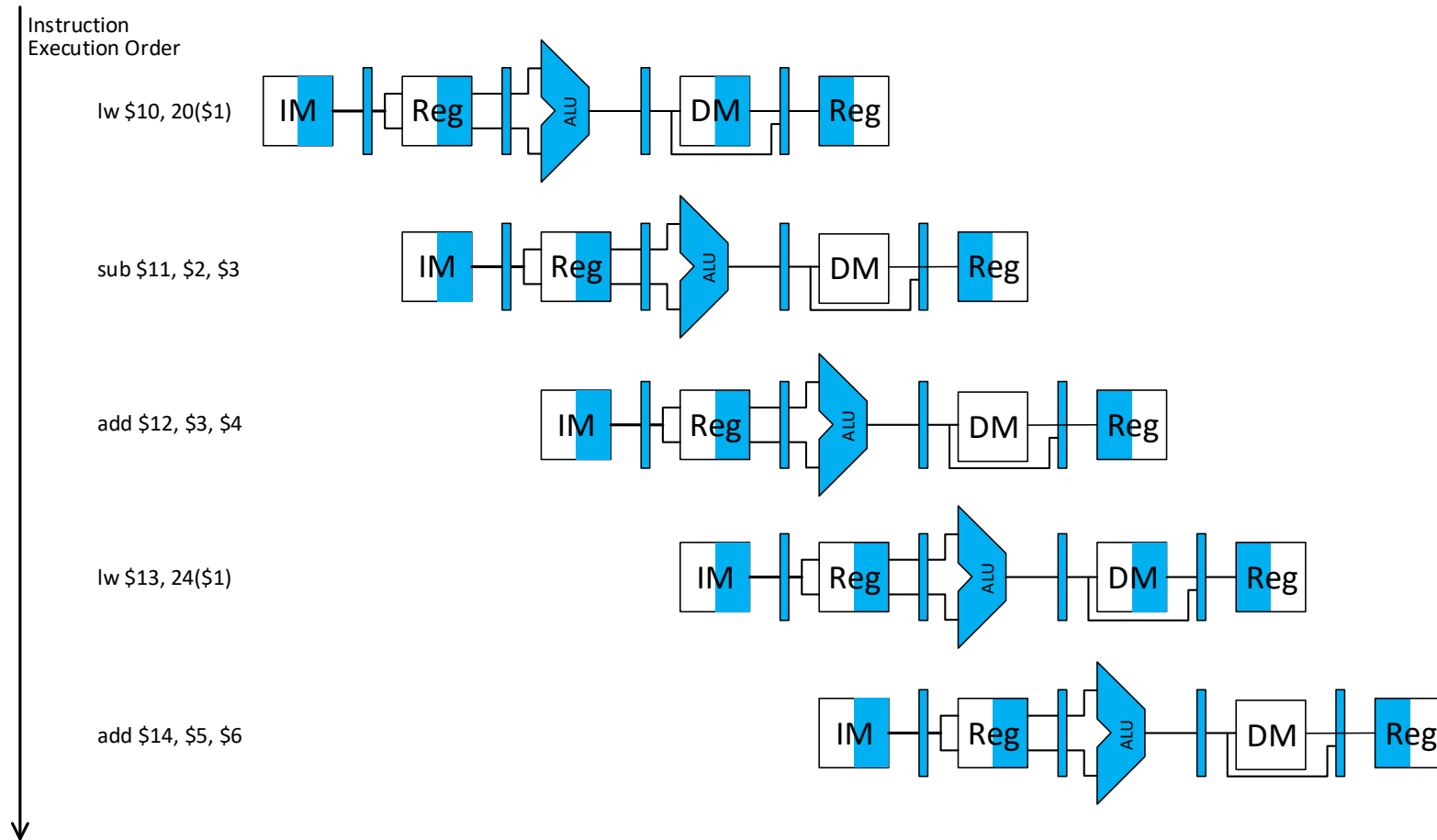
# Multi-clock-cycle Pipeline Diagram of Above Instructions with Pipeline Registers




# Identification of Control Lines

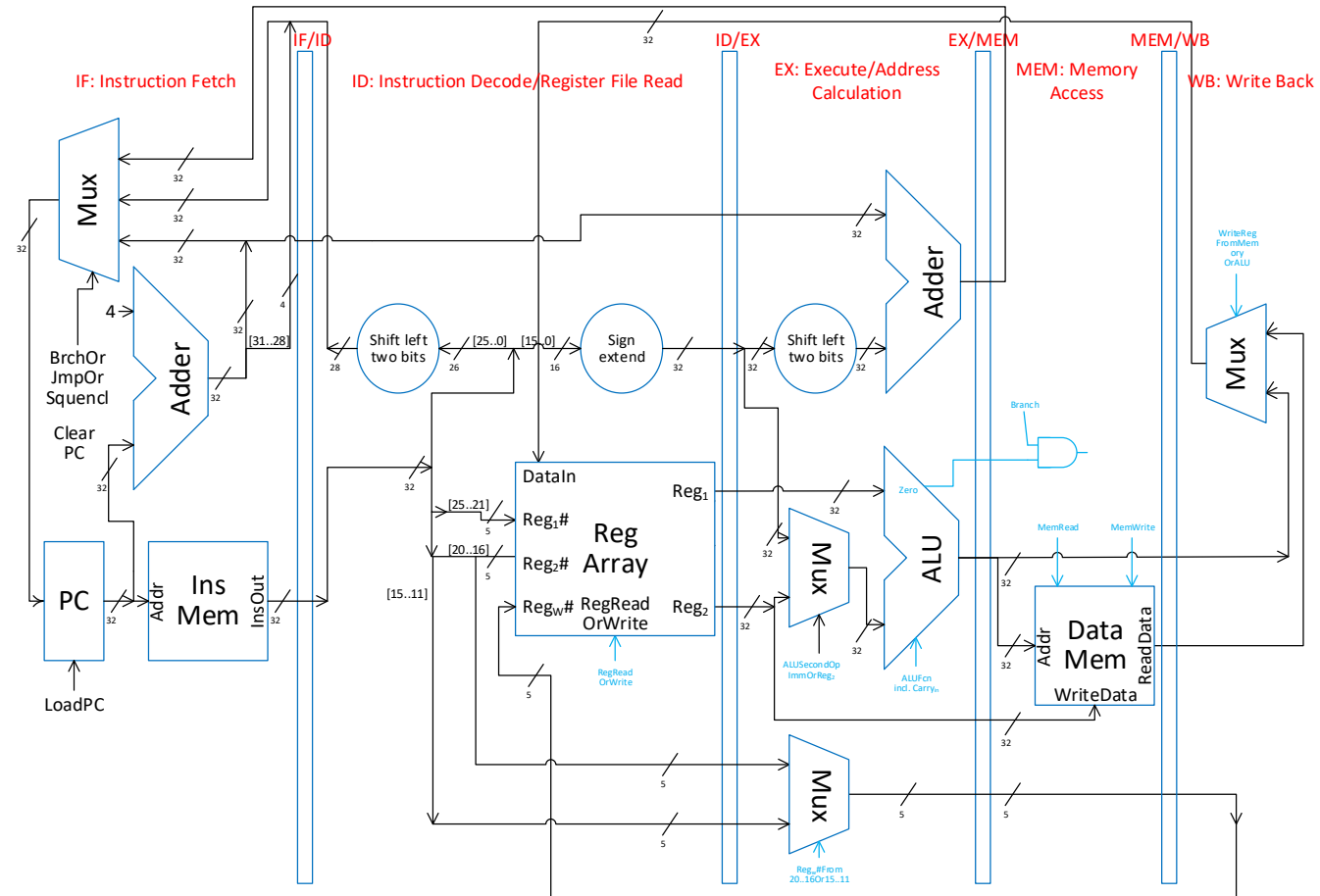


# Problem with Control Lines

- Each instruction at each stage of the pipeline needs to have its specific control lines asserted
- Difficult problem to manage the state of each instruction in each stage
  
- However, what if we stage the control lines with the pipelined data!

# Pipelined Control Summary

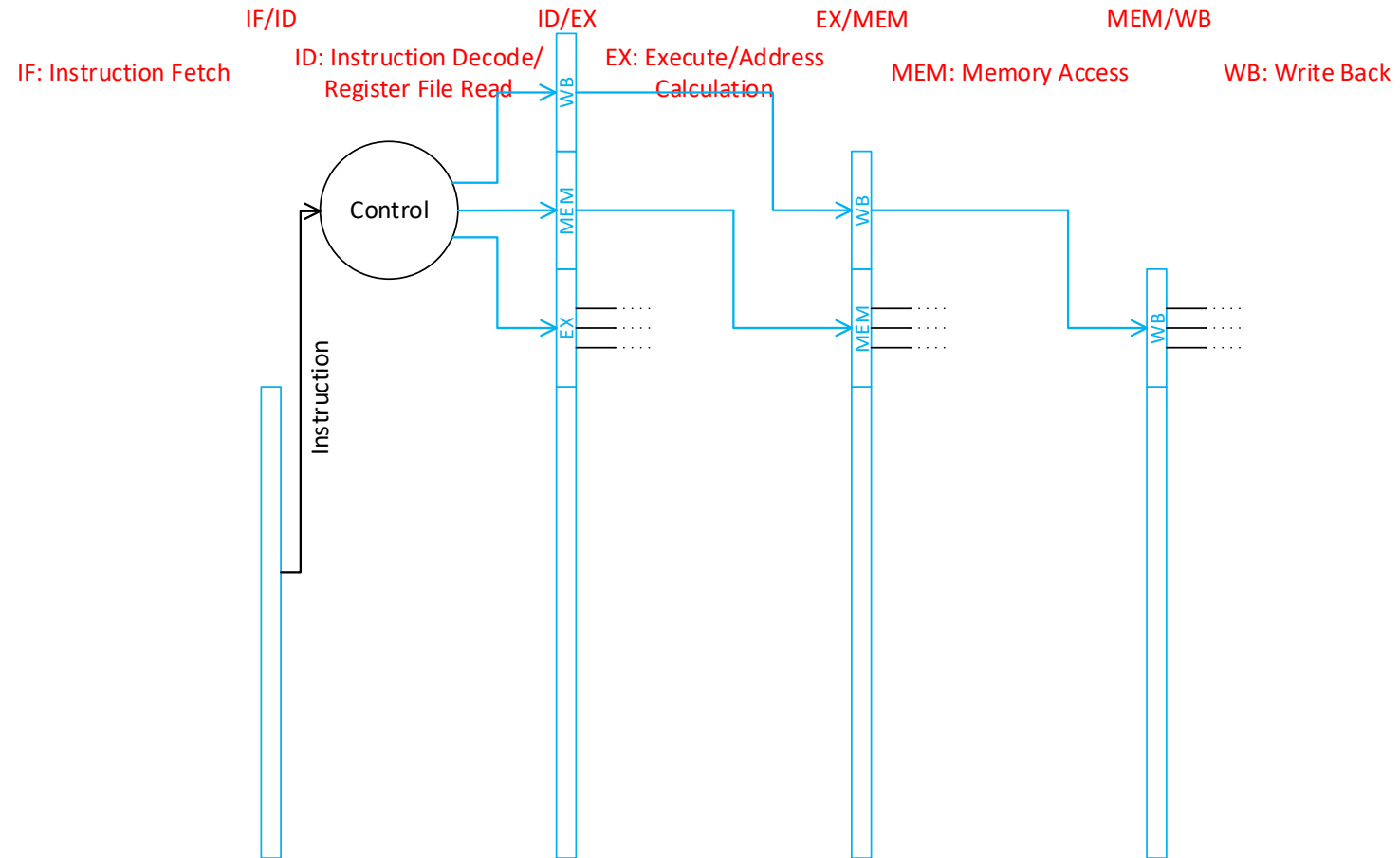

# Pipelined Control Detail

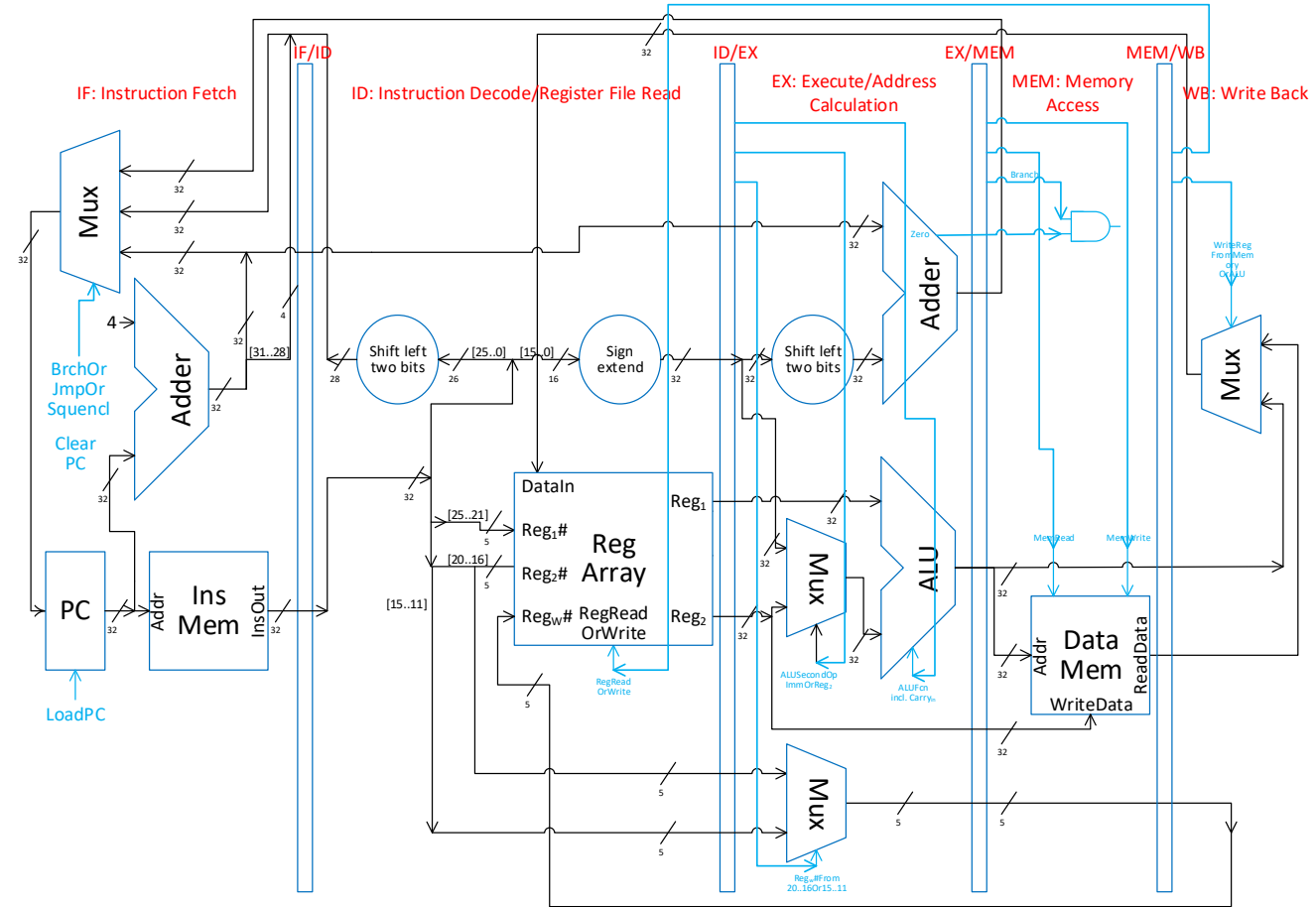

# Sequence of Instructions with Dependencies

- Pipelined execution of a sequence of five instructions with dependencies:

sub    \$2, \$1, \$3


and    \$12, \$2, \$5

or     \$13, \$6, \$2


add    \$14, \$2, \$2

sw     \$15, 100(\$2)
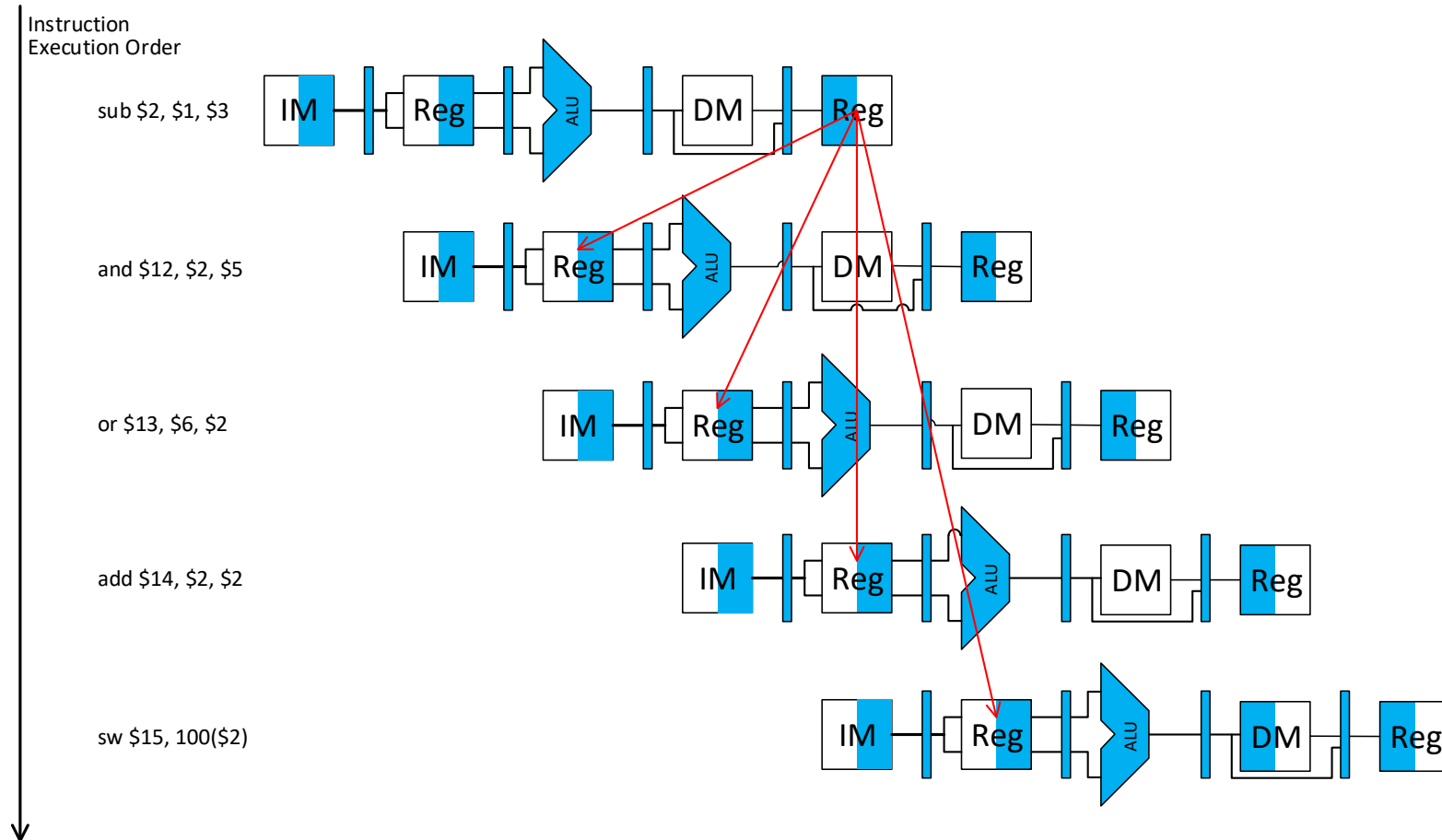
# Multi-clock-cycle Pipeline Diagram of Above Instructions with Dependencies


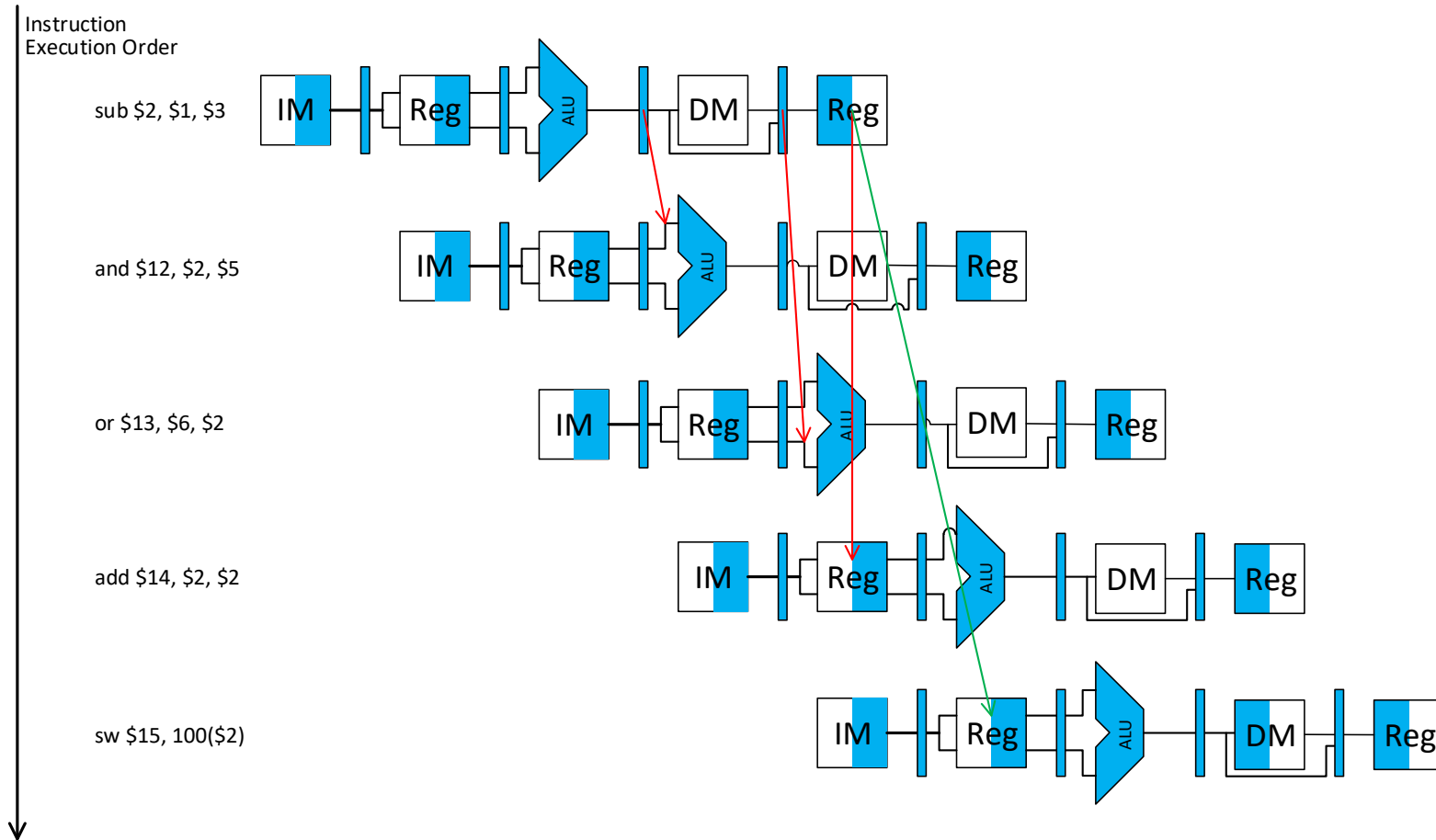
# Multi-clock-cycle Pipeline Diagram of Above Instructions with Dependencies & Forwarding





# Forwarding

- It is the responsibility of the Forwarding Unit to determine how to forward available values to where they are used

# Sequence of Instructions with Hazards & Stalls

- Pipelined execution of a sequence of five instructions with dependencies:

lw     \$2, 20(\$1)


and    \$4, \$2, \$5

or     \$8, \$2, \$6


add    \$9, \$4, \$2

slt    \$1, \$6, \$7
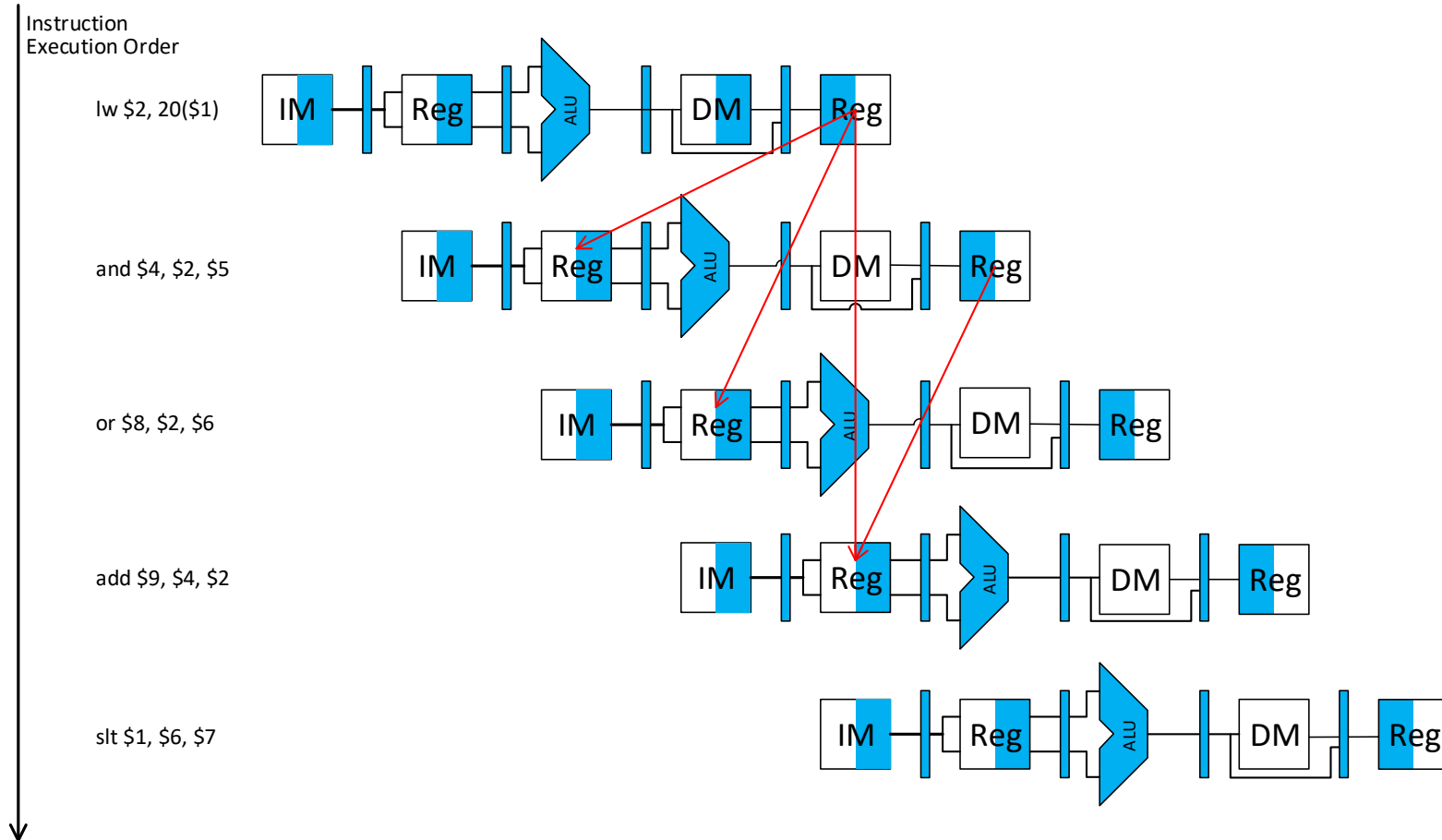
# Multi-clock-cycle Pipeline Diagram of Above Instructions with Hazards & Stalls


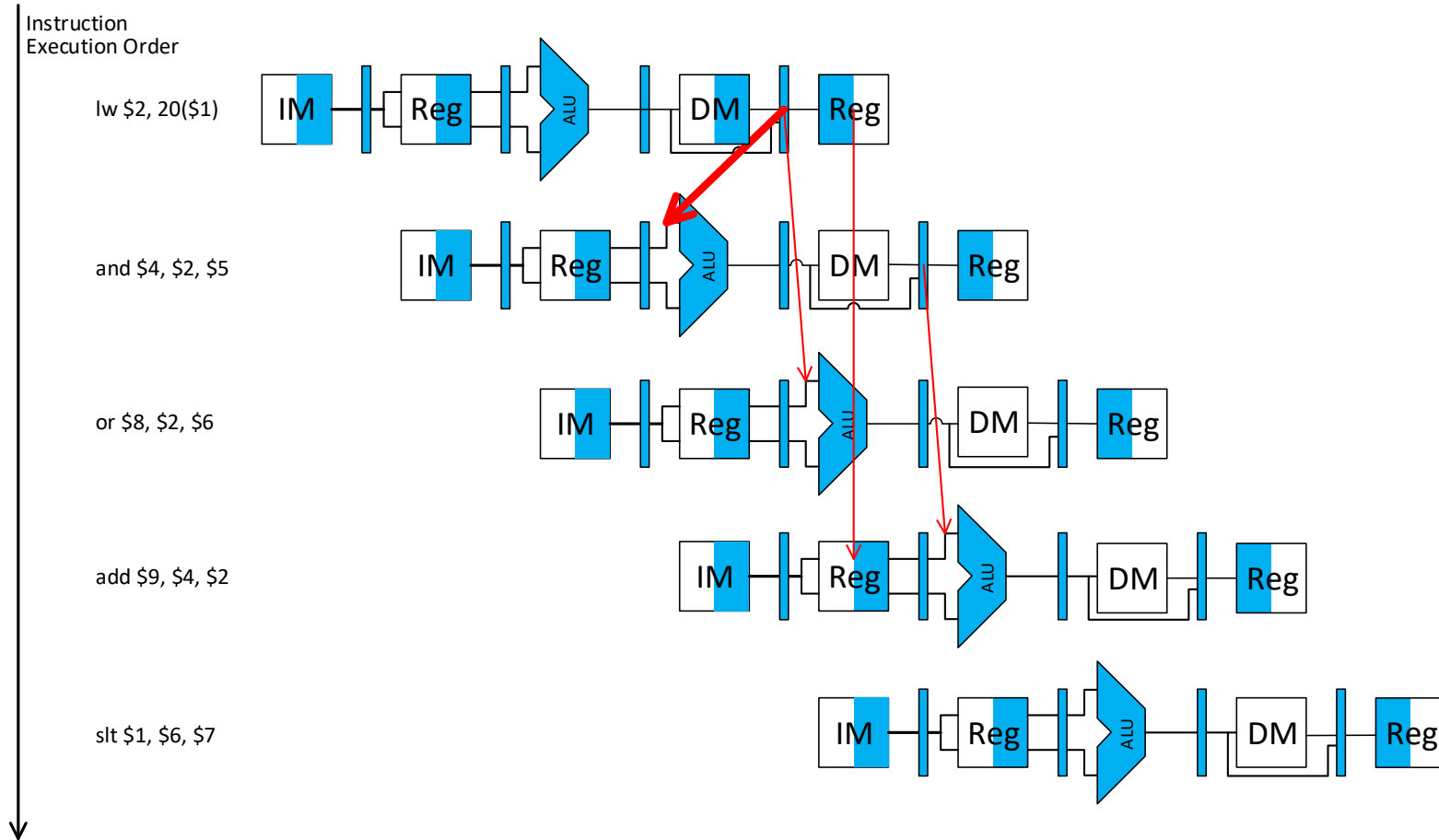
# Multi-clock-cycle Pipeline Diagram of Above Instructions with Hazards & Stalls & Forwarding



# Forwarding Does Not Solve All Our Problems

- We really need the value of **\$2** from  
    **lw \$2, 20(\$1)**  
in  
    **and \$4, \$2, \$5**  
before it is available
- This can't be corrected by using forwarding
- We need to delay the execution of **and \$4, \$2, \$5** for one clock cycle until **\$2** is available

# Hazard Detection Unit

- It is the responsibility of the Hazard Detection Unit to determine if a stall is required
- The Hazard Detection Unit inserts bubbles
- A bubble causes the CPU to perform no operation
  - We refer to this as a nop (pronounced: no op)

# Multi-clock-cycle Pipeline Diagram of Above Instructions with Hazards & Stalls Inserted

